

Part 3

Mutual Inductance



Main Outlines

- ☐ Review of self inductance
- ☐ Concept of mutual inductance
- ☐ Mutual inductance in terms of self inductance
- ☐ Polarity of the mutually induced voltages (**Dot Convention**)
- ☐ Procedure for determining dot marking
- ☐ Use of dot markings in circuit analysis
- ☐ Energy calculations




Magnetically Coupled Circuits

- When two loops with or **without contacts** between them **affect each other** through the magnetic field generated by one of them, it called ***magnetically coupled***
- **Example: transformer**
 - ✓ An electrical device designed on the basis of the concept of magnetic coupling
 - ✓ Used magnetically coupled coils to transfer energy from one circuit to another




Transformers and Power Transmission

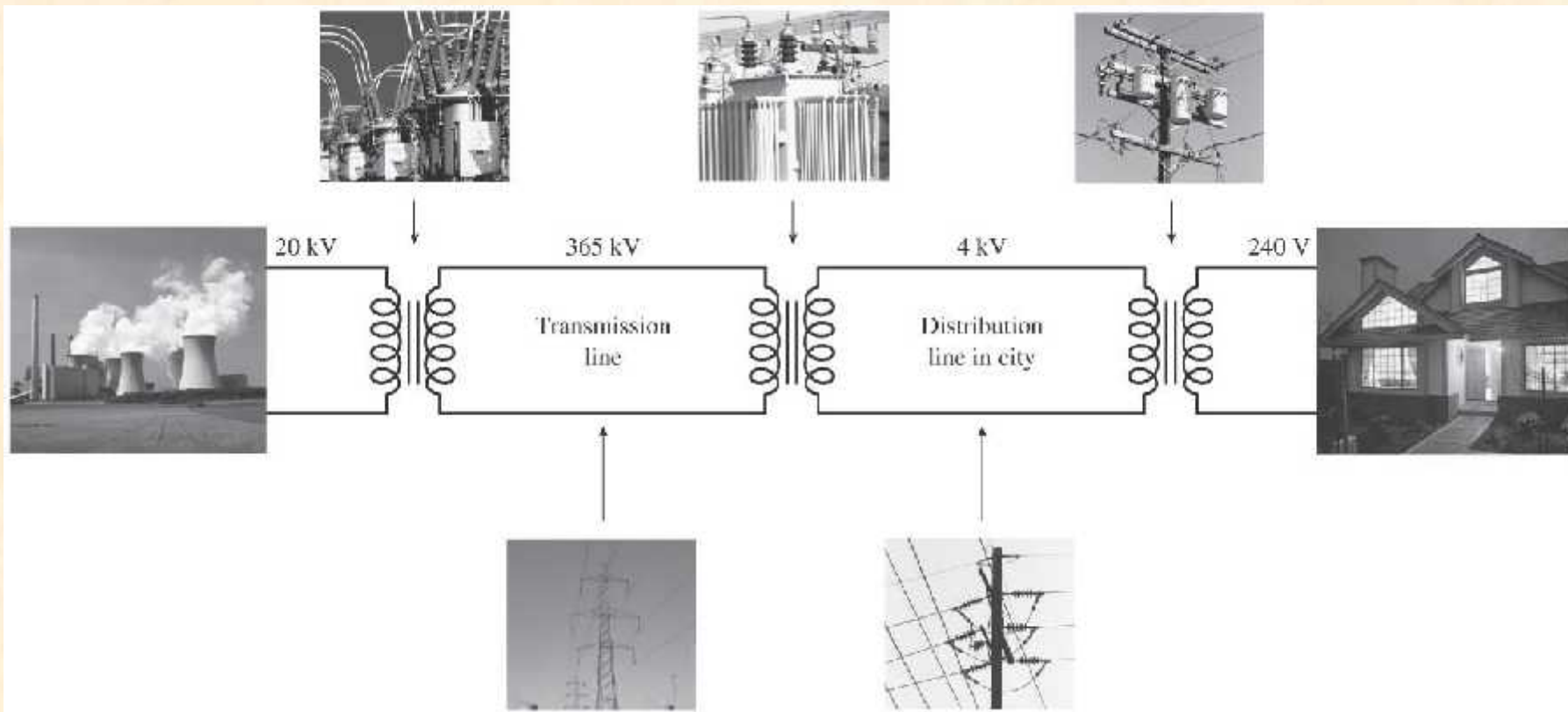- Electric power is most efficiently transmitted at high voltages.
 - This reduces I^2R energy losses in the power lines.
 - But most end uses require lower voltages.
 - Transformers accomplish voltage changes throughout the power grid.




Magnetic Field

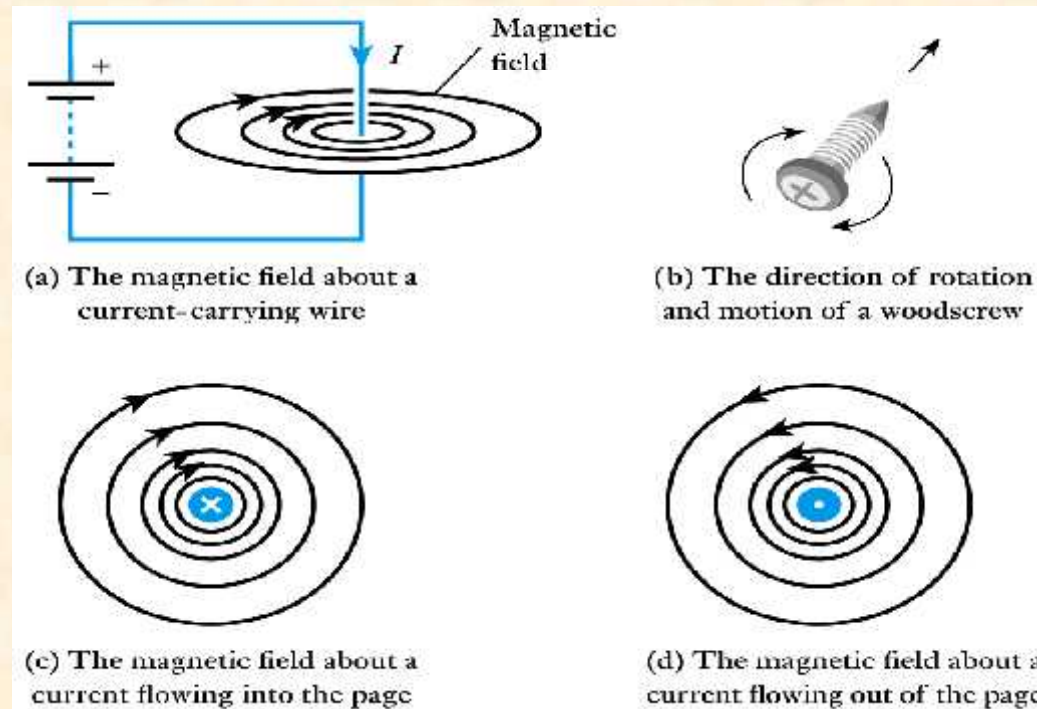
- A wire carrying a current I causes a **magneto-motive force** (**m.m.f**) F
 - this produces a **magnetic field**
 - F has units of Amperes
 - for a single wire F is equal to I



Magnetic Field

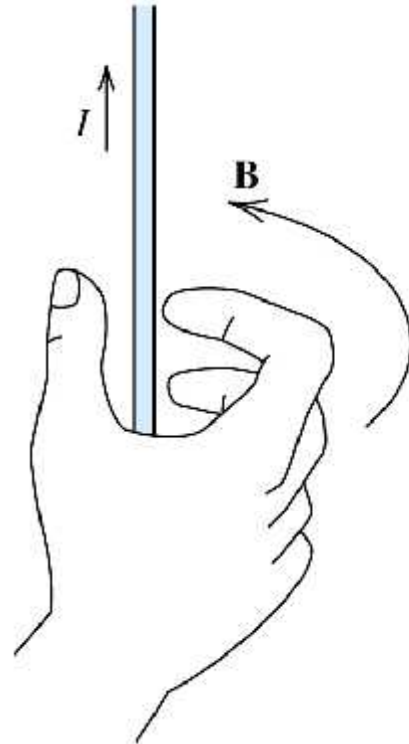

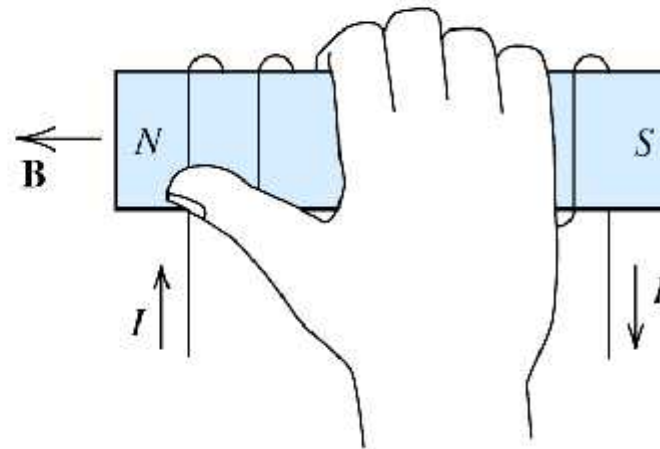(a) If a wire is grasped with the thumb pointing in the current direction, the fingers encircle the wire in the direction of the magnetic field



(b) If a coil is grasped with the fingers pointing in the current direction, the thumb points in the direction of the magnetic field inside the coil

Right-Hand Rule



Magnetic Reluctance

- In a *resistive circuit*, the resistance is a measure of how the circuit opposes the flow of electricity
- In a *magnetic circuit*, the **reluctance**, \mathfrak{R} is a measure of how the circuit opposes the flow of magnetic flux

✓ In a resistive circuit $R = V/I$

✓ In a magnetic circuit $\mathfrak{R} = \frac{F}{\Phi}$

▪ The units of reluctance are amperes per weber (A/ Wb)

▪ The magnetic **Permeance** is given by: $= \frac{1}{\mathfrak{R}}$



Flux Linkages and Faraday's Law

□ The flux linking a coil with N turns: $\lambda = N \Phi$

□ Faraday's law of magnetic induction: $e = \frac{d\lambda}{dt}$



□ The voltage induced in a coil whenever its flux linkages are changing.

□ Changes occur from:

- Magnetic field changing in time
- Coil moving relative to magnetic field



Faraday's Law

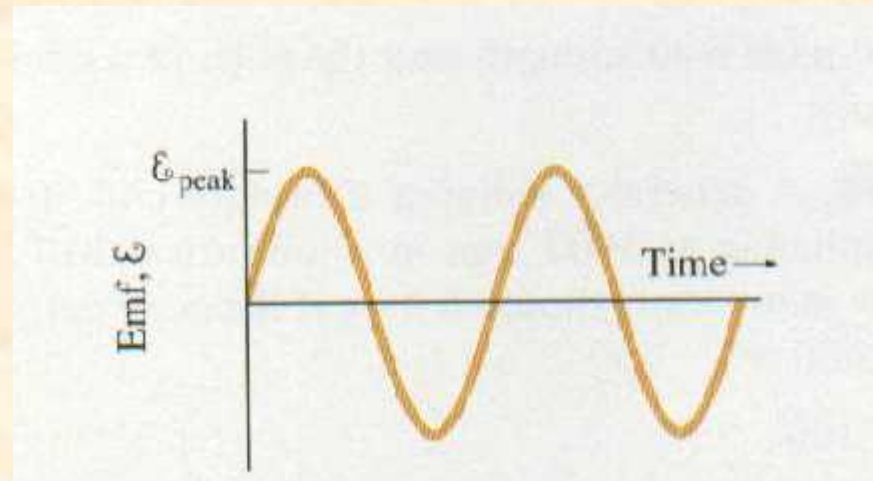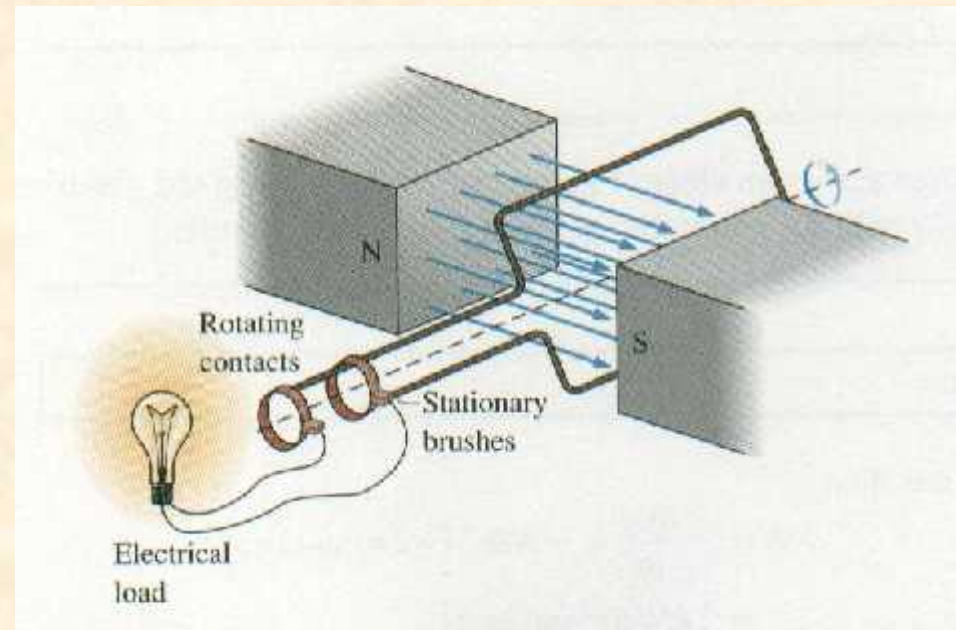


Lenz's Law

□ Lenz's law states that the **polarity** of the induced voltage is such that the voltage would produce a current (through an external resistance) that **opposes** the original change in flux linkages.

- The current in a conductor, as a result of an induced voltage, is such that the magnetic flux due to it is opposite to the magnetic flux that caused the induced voltage




Lenz's Law

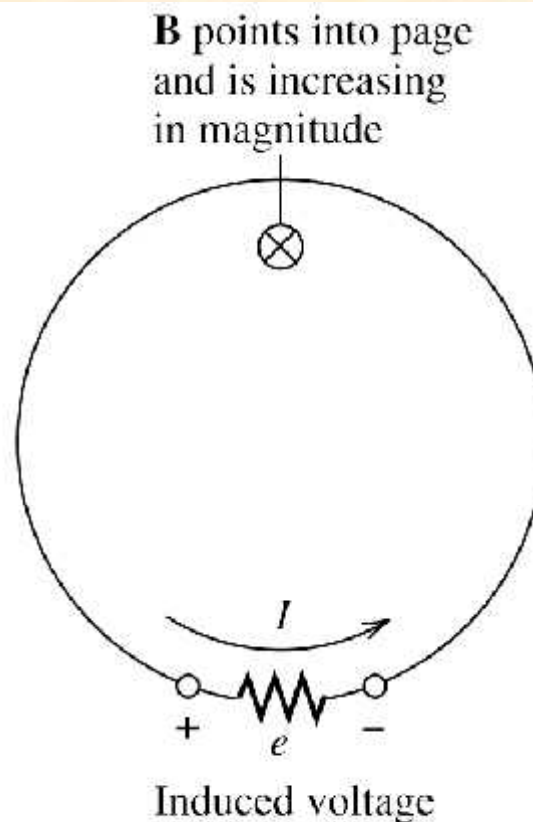

When the flux linking a coil changes, a voltage is induced in the coil. The polarity of the voltage is such that if a circuit is formed by placing a resistance across the coil terminals, the resulting current produces a field that tends to oppose the original change in the field.



Lenz's Law

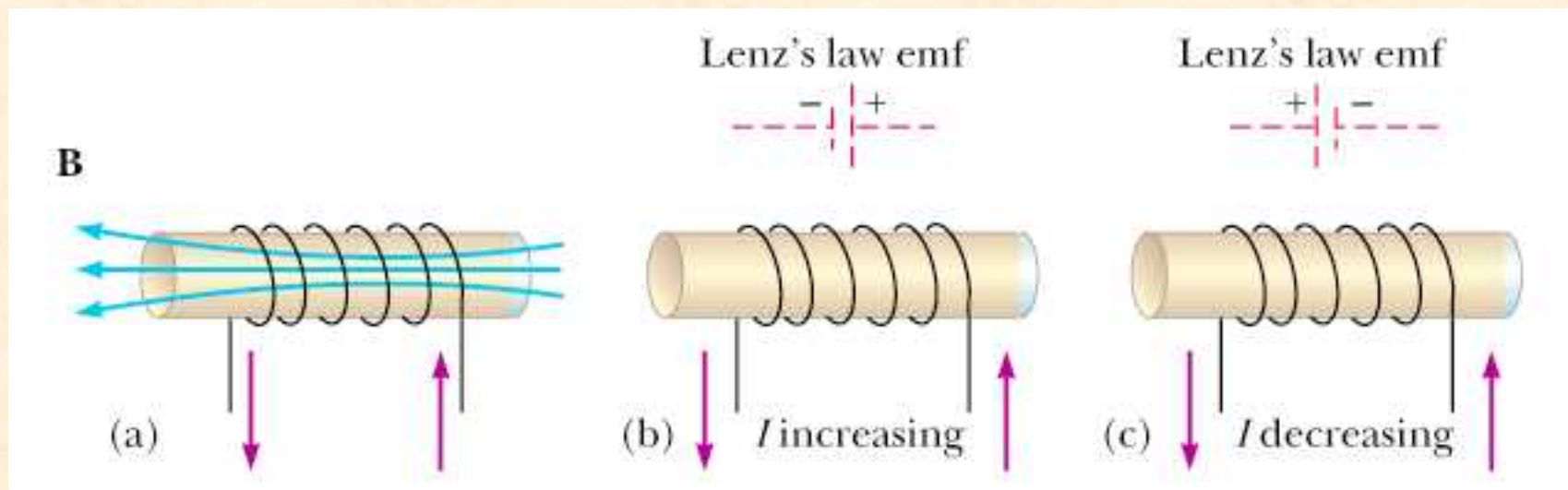

- When I changes, an emf is induced in the coil
- If I is **increasing** (and therefore increasing the flux through the coil), then the induced emf will set up a magnetic field to **oppose** the **increase** in the magnetic flux in the direction shown.
- If I is **decreasing**, then the induced emf will set up a magnetic field to **oppose** the **decrease** in the magnetic flux.



Self and Mutual Inductance

□ 1 coil (inductor)


- Single solenoid has only self-inductance (L)

□ 2 coils (inductors)

- 2 solenoids have self-inductance (L) & Mutual-inductance (M)



Self Inductance

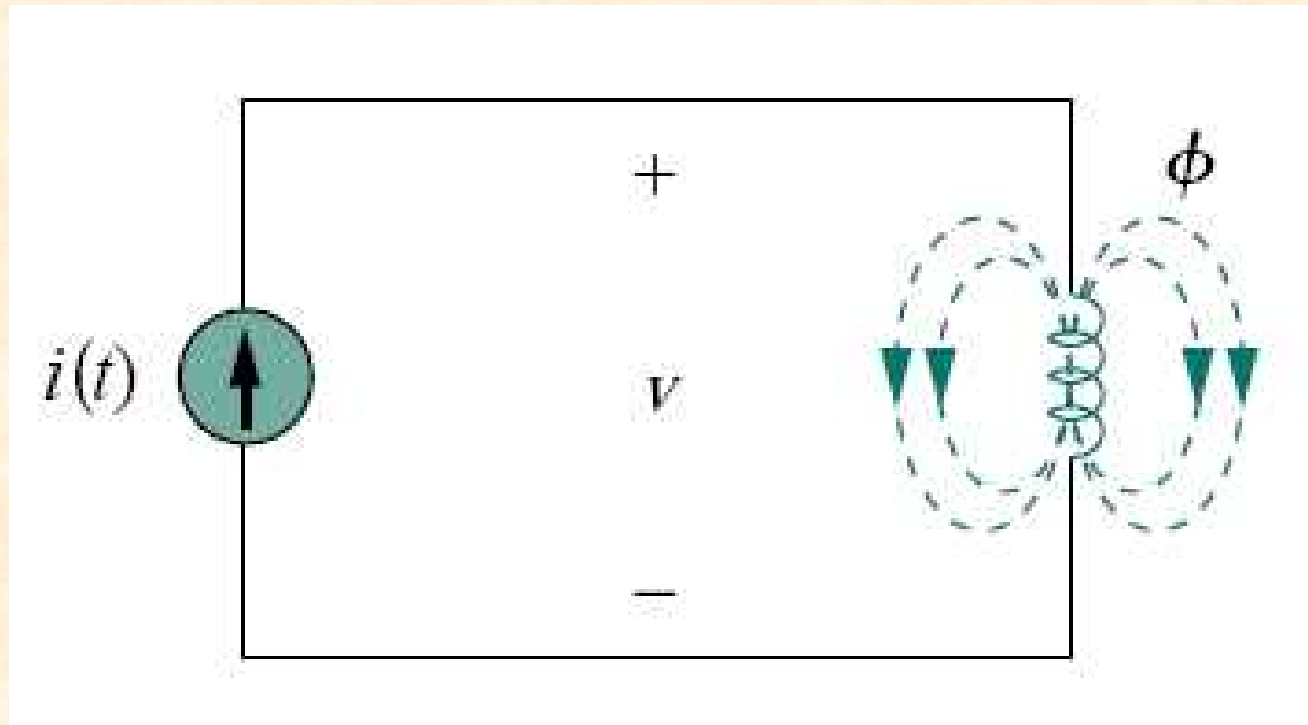

- ✓ A coil with N turns produced $\phi = \text{magnetic flux}$
- ✓ Only has self inductance, L




Self Inductance

- It called **self inductance** because it relates the voltage induced in a coil by a time varying current in the same coil
- Consider a single inductor with **N** number of turns when current, **i** flows through the coil, a magnetic flux, is produces around it

$$W = \frac{(N i)}{\mathfrak{R}} = (N i)$$

$$\} = N W = N \frac{(N i)}{\mathfrak{R}}$$
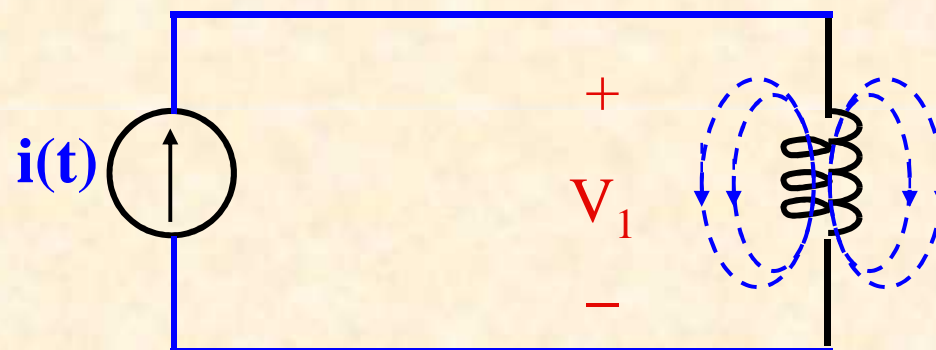
$$\} = \left(\frac{N^2}{\mathfrak{R}} \right) i = \left(N^2 \right) i$$



$$L = \frac{N^2}{\mathfrak{R}} = N^2$$

$$\} = N W = L i$$



Self Inductance

- According to Faraday's Law, the voltage, (v) induced in the coil is proportional to (N) number of turns and rate of change of the magnetic flux, ;

$$v = N \frac{d\Phi}{dt}$$

- In addition, the induced voltage, (v) can be written in terms of the self inductance, (L) and rate of change of the current, (i);

$$v = L \frac{di}{dt}$$



Self Inductance (another form)

$$v = N \frac{dW}{dt}$$


$$\frac{dW}{dt} = \frac{dW}{di} \frac{di}{dt}$$

$$v = N \frac{dW}{di} \frac{di}{dt} \quad \text{or} \quad v = L \frac{di}{dt}$$

$$L = N \frac{dW}{di} \quad (\text{H})$$



Self Inductance (conclusions)

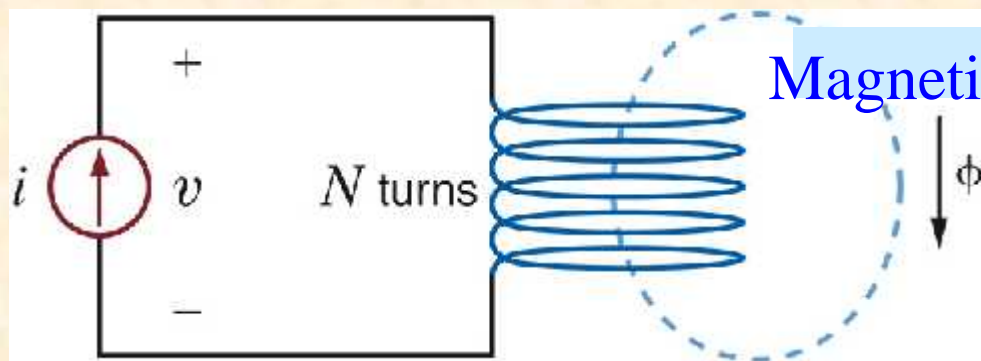

Magnetic field

$$\lambda = N\Phi$$


Total magnetic flux linked by N -turn coil

$$v = \frac{d\lambda}{dt}$$

Faraday's Induction Law

$$\lambda = Li$$

Ampere's Law

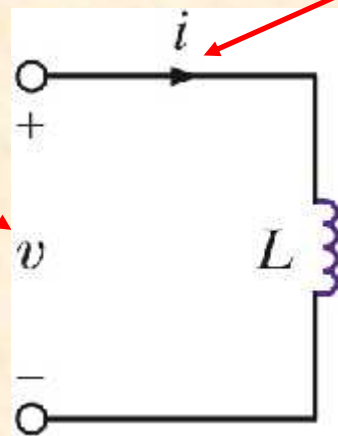


$$v = L \frac{di}{dt}$$

Ideal Inductor

$$L = \frac{N^2}{\mathfrak{R}} = N^2$$




Resistor and Inductor

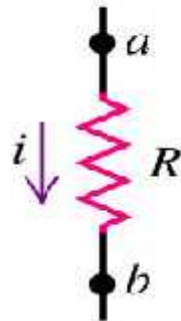

$$V_{ab} = iR$$

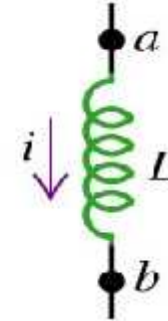(a) Resistor with current i flowing from a to b :
potential drops from a to b

Potential difference across a resistor depends on the current



$$V_{ab} = L \frac{di}{dt}$$

(b) Inductor with current i flowing from a to b :

- If $di/dt > 0$: potential drops from a to b
- If $di/dt < 0$: potential increases from a to b
- If i is constant ($di/dt = 0$): no potential difference


Potential difference across an inductor depends on the **rate of change** of the current



Inductor

- The inductance of a coil depends on its dimensions and the materials around which it is formed


$$L = \frac{\mu_0 AN^2}{l}$$

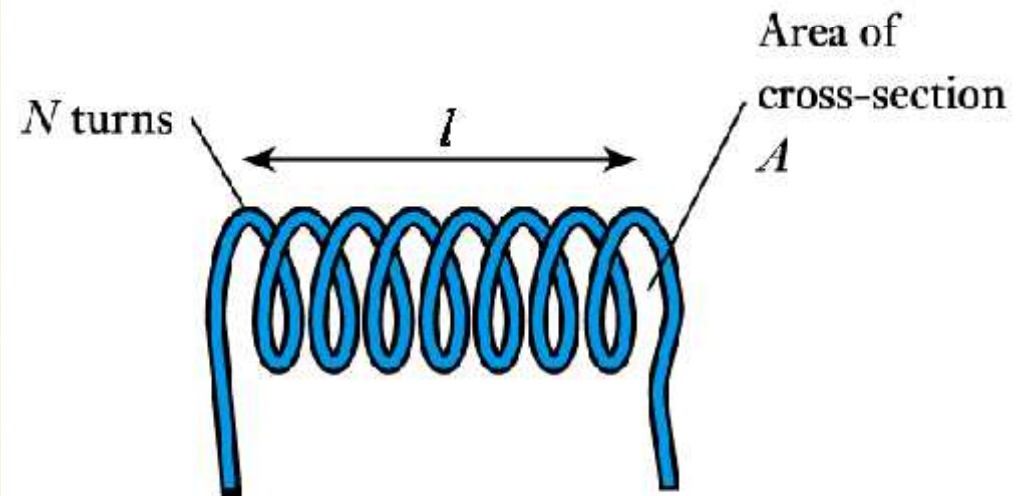

(a) An air-filled coil



Types of Inductors

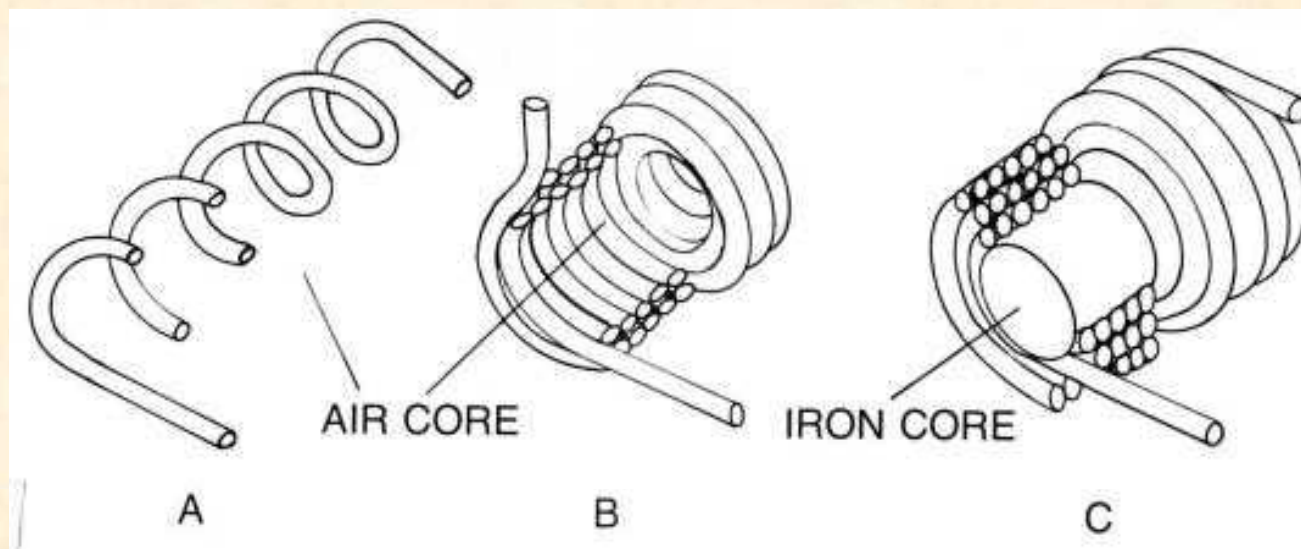

$$L = \frac{\mu_0 \mu_r A N^2}{l} = \frac{N^2}{\mathfrak{R}} = N^2$$

$$\mathfrak{R} = \frac{1}{\frac{l}{\mu_0 \mu_r A}}$$





Factors Affecting Inductance of Coils

- ✓ **Numbers of Turns-** Inductance varies directly with the square of the number of turns
- ✓ **Permeability of Core-** Inductance varies directly with the permeability of the core
- ✓ **Cross-sectional Area of Core-** Inductance varies directly with the cross-sectional area of the core
- ✓ **Length of Core-** Inductance varies inversely with the length of the core




Mutual Inductance

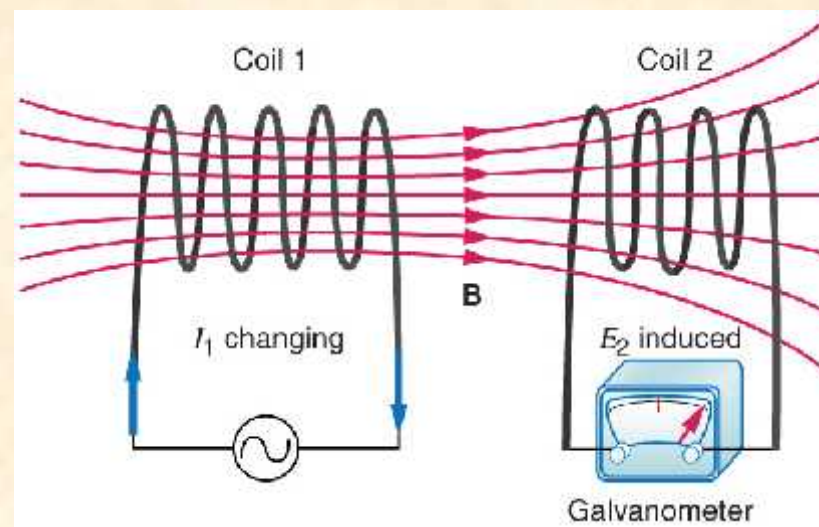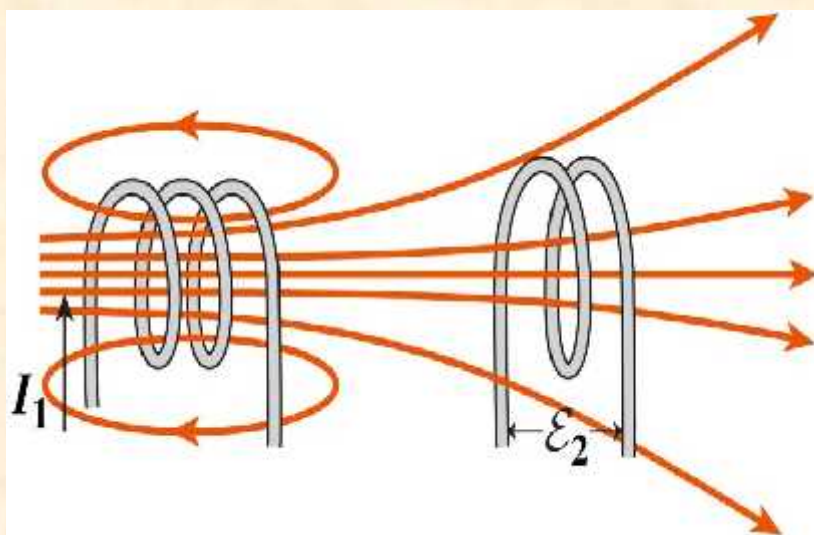- When two inductors or coils are in close proximity to each other, magnetic flux caused by current in one coil links with the other coil, therefore producing the induced voltage



Mutual Inductance

- ❑ **Mutual inductance** occurs when a changing current in one circuit results, via changing magnetic flux, in an induced emf and thus a current in an adjacent circuit
- ❑ The coils are said to have mutual inductance M , which can either add or subtract from the total inductance depending on if the fields are aiding or opposing
- ❑ **Mutual inductance** is the ability of one inductor to induce a voltage across a neighboring inductor

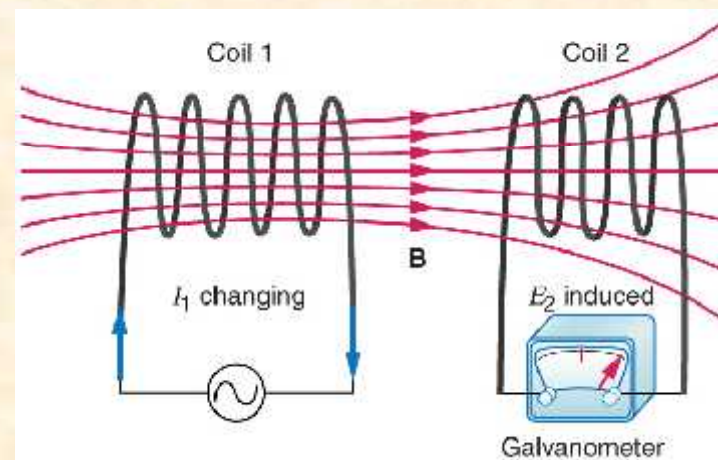


Mutual Inductance

Consider the following two cases:

□ Case 1:

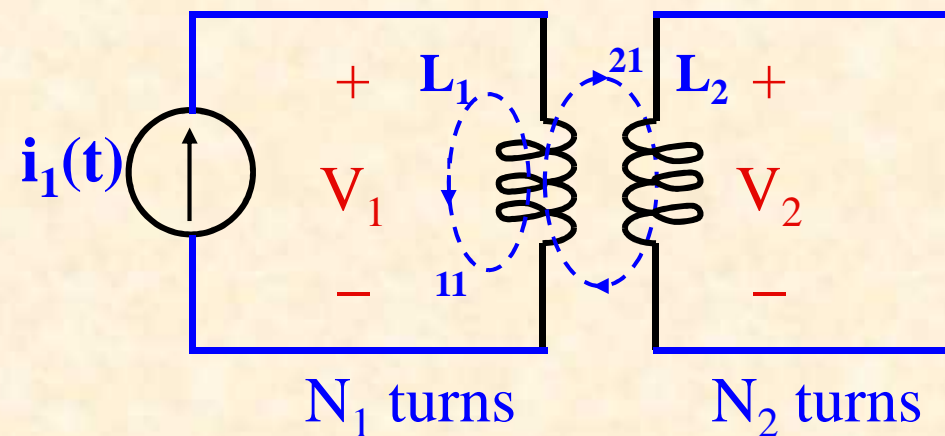two coil with self – inductances L_1 and L_2 which are in close proximity which each other. Coil 1 has N_1 turns, while coil 2 has N_2 turns



Mutual Inductance

➤ Magnetic flux Φ_1 from coil 1 has two components;

* Φ_{11} links only coil 1

* Φ_{21} links both coils

✓ Hence; $\Phi_1 = \Phi_{11} + \Phi_{21}$

where

$$W_1 = \frac{N_1 i_1}{\mathcal{R}_1} = N_1 i_1 \Phi_1$$

Total flux

$$\Phi_1 = \Phi_{11} + \Phi_{21}$$

Leakage flux

$$W_{11} = \frac{N_1 i_1}{\mathcal{R}_{11}} = N_1 i_1 \Phi_{11}$$

$$W_{21} = \frac{N_1 i_1}{\mathcal{R}_{21}} = N_1 i_1 \Phi_{21}$$

**Magnetizing
(Mutual) flux**



Mutual Inductance

➤ Thus; the voltage induces in coil 1

$$v_1 = N_1 \frac{dW_1}{dt}$$

$$v_1 = N_1 \frac{d}{dt} (W_{11} + W_{21})$$

$$v_1 = N_1^2 \left(L_{11} + M_{21} \right) \frac{di_1}{dt}$$

$$v_1 = \left(N_1^2 L_{11} \right) \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$



Mutual Inductance

- ✓ The Voltage induces in coil 2

$$v_2 = N_2 \frac{dw_{21}}{dt}$$

$$w_{21} = \frac{N_1 i_1}{\mathfrak{R}_{21}} = N_1 i_1 \quad 21$$

$$v_2 = N_2 N_1 \quad 21 \frac{di_1}{dt} = M_{21} \frac{di_1}{dt}$$


Subscript 21 in M_{21}
means the mutual
inductance on coil
2 due to coil 1

$$M_{21} = \frac{N_2 N_1}{\mathfrak{R}_{21}} = N_2 N_1 \quad 21$$



Mutual Inductance

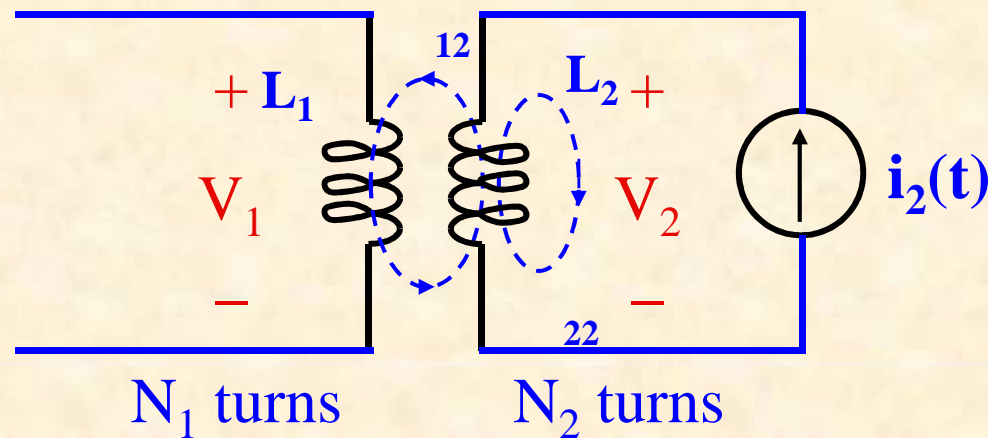□ **Case 2:** Same circuit but let current i_2 flow in coil 2.



✓ The magnetic flux Φ_{22} from coil 2 has two components:

* Φ_{22} links only coil 2

* Φ_{12} links both coils



Mutual Inductance

➤ Hence; $\Phi_2 = \Phi_{22} + \Phi_{12}$

where

$$\Phi_2 = \frac{N_2 i_2}{\mathcal{R}_2} = N_2 i_2 \quad 2$$

Total flux

$$\Phi_2 = \Phi_{22} + \Phi_{12}$$

Leakage flux

$$\Phi_{22} = \frac{N_2 i_2}{\mathcal{R}_{22}} = N_2 i_2 \quad 22$$

$$\Phi_{12} = \frac{N_2 i_2}{\mathcal{R}_{12}} = N_2 i_2 \quad 12$$

**Magnetizing
(Mutual) flux**



Mutual Inductance

✓ Thus; the voltage induced in coil 2

$$v_2 = N_2 \frac{dW_2}{dt}$$

$$v_2 = N_2 \frac{d}{dt} (W_{22} + W_{12})$$

$$v_2 = N_2^2 \left(L_{22} + L_{12} \right) \frac{di_2}{dt}$$

$$v_2 = \left(N_2^2 L_{22} + N_2^2 L_{12} \right) \frac{di_2}{dt} = L_2 \frac{di_2}{dt}$$



Mutual Inductance

- ✓ The Voltage induces in coil 1

$$v_1 = N_1 \frac{dw_{12}}{dt}$$

$$w_{12} = \frac{N_2 i_2}{\mathcal{R}_{12}} = N_2 i_2 \quad 12$$

$$v_1 = N_1 N_2 \frac{di_2}{dt} = M_{12} \frac{di_2}{dt}$$

Subscript 12 in M_{12}
means the mutual
inductance on coil
1 due to coil 2

$$M_{12} = \frac{N_1 N_2}{\mathcal{R}_{12}} = N_1 N_2 \quad 12$$



Mutual Inductance

□ For a linear system

$$\mathcal{R}_{21} = \mathcal{R}_{12}$$

$$M_{21} = M_{12} = M$$

➤ Mutual inductance **M** is measured in Henrys (H)



Mutual Inductance (another form)

➤ Case 1:

$$v_1 = N_1 \frac{dW_1}{di_1} \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$

$$v_2 = N_2 \frac{dW_{21}}{di_1} \frac{di_1}{dt} = M_{21} \frac{di_1}{dt}$$

➤ Case 2:

$$v_2 = N_2 \frac{dW_2}{di_2} \frac{di_2}{dt} = L_2 \frac{di_2}{dt}$$

$$v_1 = N_1 \frac{dW_{12}}{di_2} \frac{di_2}{dt} = M_{12} \frac{di_2}{dt}$$

